Robotics with Arduino

Intro to Circuits



Leah Buechley









Circuits





What is a Circuit?

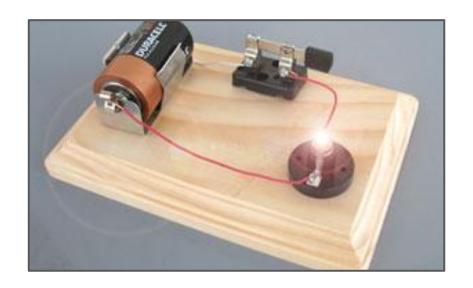


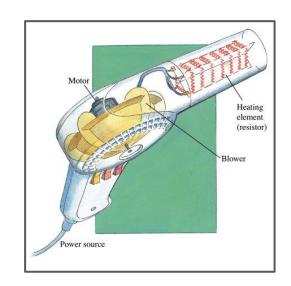





What is a Breadboard?

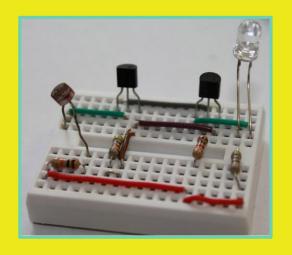
A breadboard is a tool used to prototype electronics.



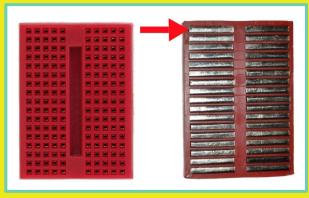

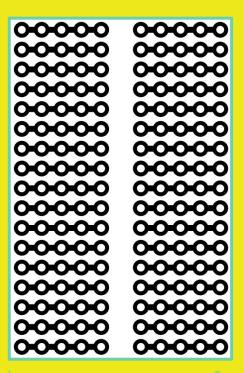



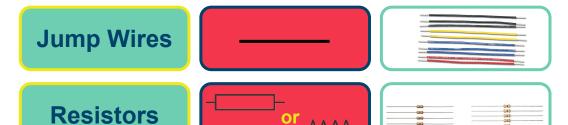


LEDs





Button

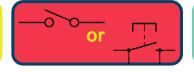



Piezo Element





Photo Transistor





Servo Motor






Components







Build This Circuit!

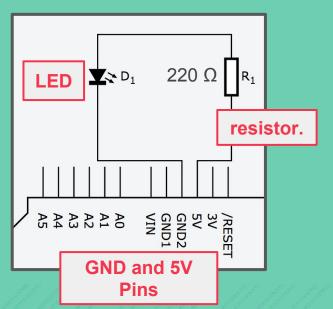
- 1. Identify the components
- 2. Plan your breadboard
- 3. Build and test



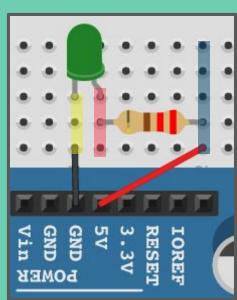

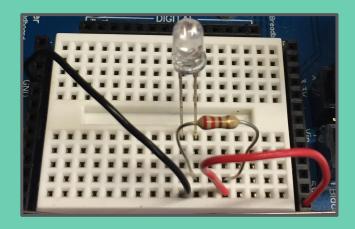





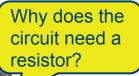

What are resistors?

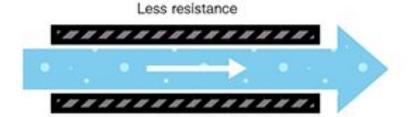The resistor slows the electricity down so the circuit doesn' t catch fire.




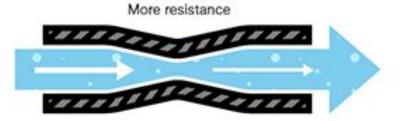






Let's try another!

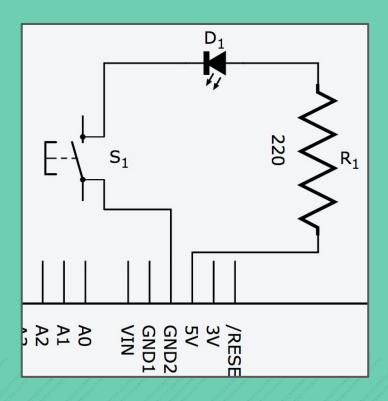

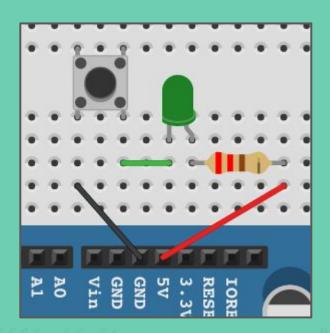- 1. Identify the components
- 2. Plan your breadboard
- 3. Build and test






Buttons




Grounded Pin	Button Pressed	LED on?
1	Pressed	
	Not Pressed	
2	Pressed	
	Not Pressed	
3	Pressed	
	Not Pressed	

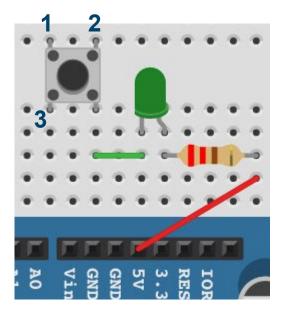




In Series Vs. In Parallel

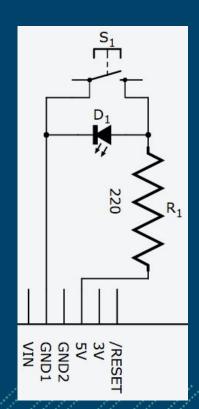







In Series Vs. In Parallel

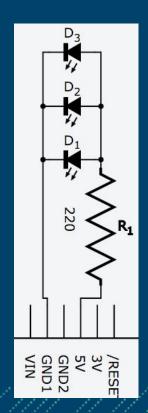


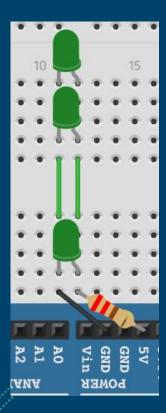



In Series Vs. In Parallel

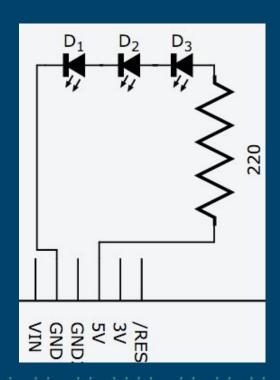

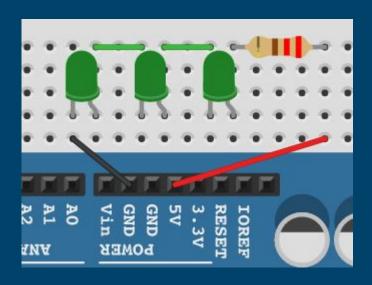



Programming with Arduino

Get your LEDs under Control!










What is an Arduino?





What is the Parallax BoE Bot?

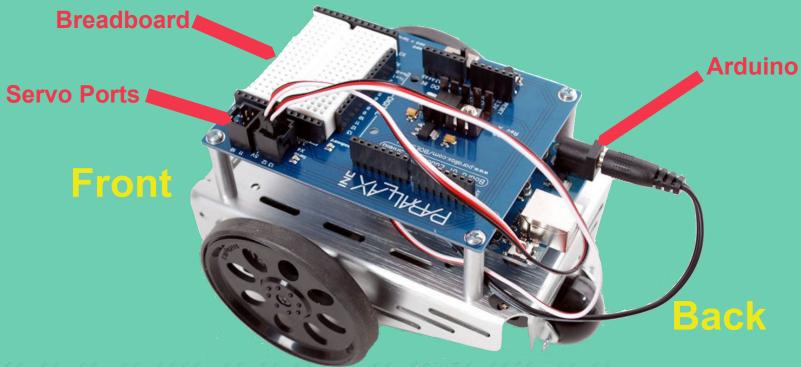



Arduino Program Layout

```
sketch_mar23a
void setup() {
 // put your setup code here, to run once:
void loop() {
 // put your main code here, to run repeatedly:
```



Functions

pinMode(pin , INPUT/OUTPUT)

digitalWrite(pin, HIGH/LOW)

delay(time)



What does this program do?

```
int LEDPIN = 4;
void setup(){
    pinMode(LEDPIN, OUTPUT);
void loop(){
   digitalWrite(LEDPIN, HIGH);
   delay(500);
   digitalWrite(LEDPIN, LOW);
   delay(1500);
```

girla who




Your Turn!


- 1. Make circuits for two LEDs to be controlled INDEPENDENTLY from pins 4 and 5.
- 2. Write a program that makes the two LEDs blink in the following way:
 - a. The LED connected to pin 4 is on when the pin 5 LED is off and they blink on for one second, off for one second.

When you complete this, create your own pattern with the LEDs!



Two LEDs

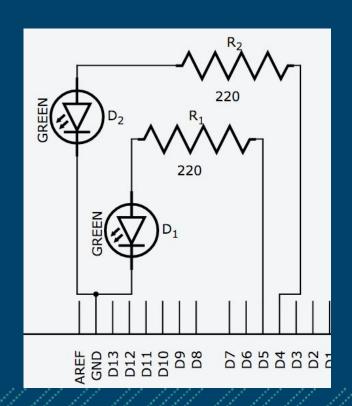


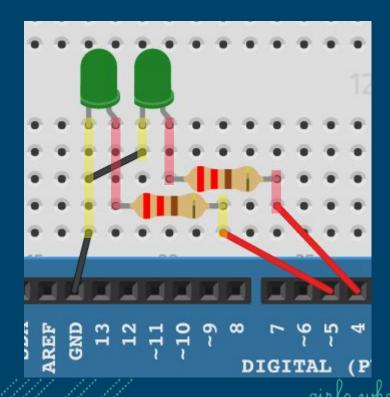

Buttons!

pinMode(4, INPUT);

digitalRead(4)

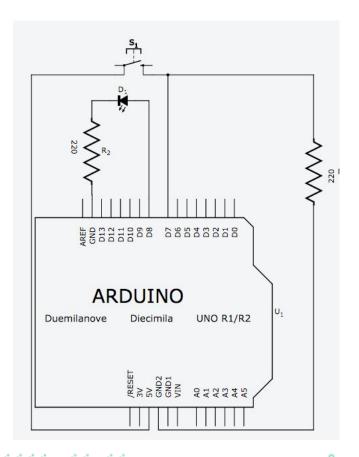



Conditionals and Boolean Operators in C++

```
if (condition) {
else if (condition) {
else {
```

- Is equal to: ==
- Is greater than: >
- Is greater than or equal to: >=
- Is less than: <
- Is less than or equal to: <=
- Is not equal to: !=
- And: &&
- Or: ||

